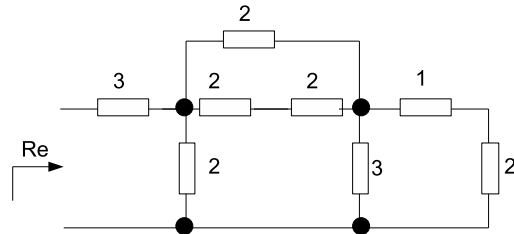


# ELK - Basics of electronics - Test 1

name: .....


index number: .....

1. Transform schematic diagram to find the value of equivalent resistance  $R_e$




2. Impedance divider  $R L$  is used as high-pass filter. Draw the schematic diagram of that filter, find transmittance (transform function) and formula describing cut-off frequency. For  $R = 1k\Omega$  and  $L = 100mH$  calculate that frequency. Draw amplitude characteristic, describe axes and state cut-off frequency. Is it lower or upper frequency ?

3. For the following circuit:

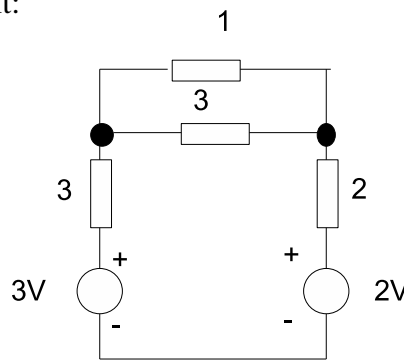

find currents in all branches. Any method can be chosen.

4. For given one-port

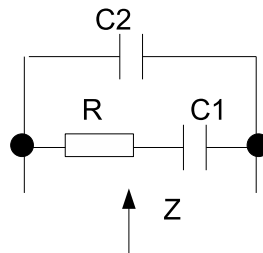

find impedance knowing, that  $C_1 = 10nF$ ,  $C_2 = 20nF$ ,  $R = 10k\Omega$  and  $\omega = 10k \frac{rad}{s}$ . Find the phase shift between voltage and current.